

CS 3468 – Homework 2

Stuart Olsen

September 22, 2014

Chapter 3

2a. (Please use the schematic symbols on page 594)

12.

19.

20. (Describe what these ICs are)

Additional Questions

The resistance of a thermistor changes according to the temperature. In the right circuit, the resistance function of the thermistor is $R_0 = 10\,000\,\Omega + 60\,\Omega^\circ\text{F}^{-1} \cdot T$. The other resistor is $R_1 = 10\,000\,\Omega$. The output voltage on R_1 is $V_0 = 3\,\text{V} \cdot \frac{R_1}{R_0 + R_1}$.

a If the room temperature is $T = 70^\circ\text{F}$, what is V_0 ?

$$\begin{aligned} V_0 &= 3\,\text{V} \cdot \frac{R_1}{R_0 + R_1} \\ &= 3\,\text{V} \cdot \frac{10\,000\,\Omega}{R_0 + 10\,000\,\Omega} \\ &= 3\,\text{V} \cdot \frac{10\,000\,\Omega}{(10\,000\,\Omega + 60\,\Omega^\circ\text{F}^{-1} \cdot T) + 10\,000\,\Omega} \\ &= 3\,\text{V} \cdot \frac{10\,000\,\Omega}{(10\,000\,\Omega + 60\,\Omega^\circ\text{F}^{-1} \cdot 70^\circ\text{F}) + 10\,000\,\Omega} \\ &= 3\,\text{V} \cdot \frac{10\,000\,\Omega}{(10\,000\,\Omega + 4200\,\Omega) + 10\,000\,\Omega} \\ &= 3\,\text{V} \cdot \frac{10\,000\,\Omega}{14\,200\,\Omega + 10\,000\,\Omega} \\ &= 3\,\text{V} \cdot \frac{10\,000\,\Omega}{24\,200\,\Omega} \\ &= \frac{30\,000}{24\,200}\,\text{V} \\ &\approx \boxed{1.24\,\text{V}} \end{aligned}$$

b If $V_0 = 1.339 \text{ V}$, what is the room temperature?

$$\begin{aligned}
 V_0 &= 3 \text{ V} \cdot \frac{R_1}{R_0 + R_1} \\
 1.339 \text{ V} &= 3 \text{ V} \cdot \frac{10\,000 \, \Omega}{(10\,000 \, \Omega + 60 \, \Omega \, ^\circ\text{F}^{-1} \cdot T) + 10\,000 \, \Omega} \\
 \frac{1.339}{30\,000} &= \frac{1 \, \Omega}{(10\,000 \, \Omega + 60 \, \Omega \, ^\circ\text{F}^{-1} \cdot T) + 10\,000 \, \Omega} \\
 \frac{30\,000}{1.339} &= \frac{(10\,000 \, \Omega + 60 \, \Omega \, ^\circ\text{F}^{-1} \cdot T) + 10\,000 \, \Omega}{1 \, \Omega} \\
 &= \frac{20\,000 \, \Omega + 60 \, \Omega \, ^\circ\text{F}^{-1} \cdot T}{1 \, \Omega} \\
 &= 20\,000 + 60 \, ^\circ\text{F}^{-1} \cdot T \\
 \frac{30\,000}{1.339} - 20\,000 &= 60 \, ^\circ\text{F}^{-1} \cdot T \\
 T &= \frac{\frac{30\,000}{1.339} - 20\,000}{60} \, ^\circ\text{F} \\
 &\approx \boxed{40.1 \, ^\circ\text{F}}
 \end{aligned}$$